

CS-235

COMPUTER ORGANIZATION
AND
ASSEMBLY LANGUAGE

ASSIGNMENT #1

Name:

Mahum Samar

CMS ID:


290647

submitted to:

Professor Mahammed Imran

PART - I

QUESTION #1

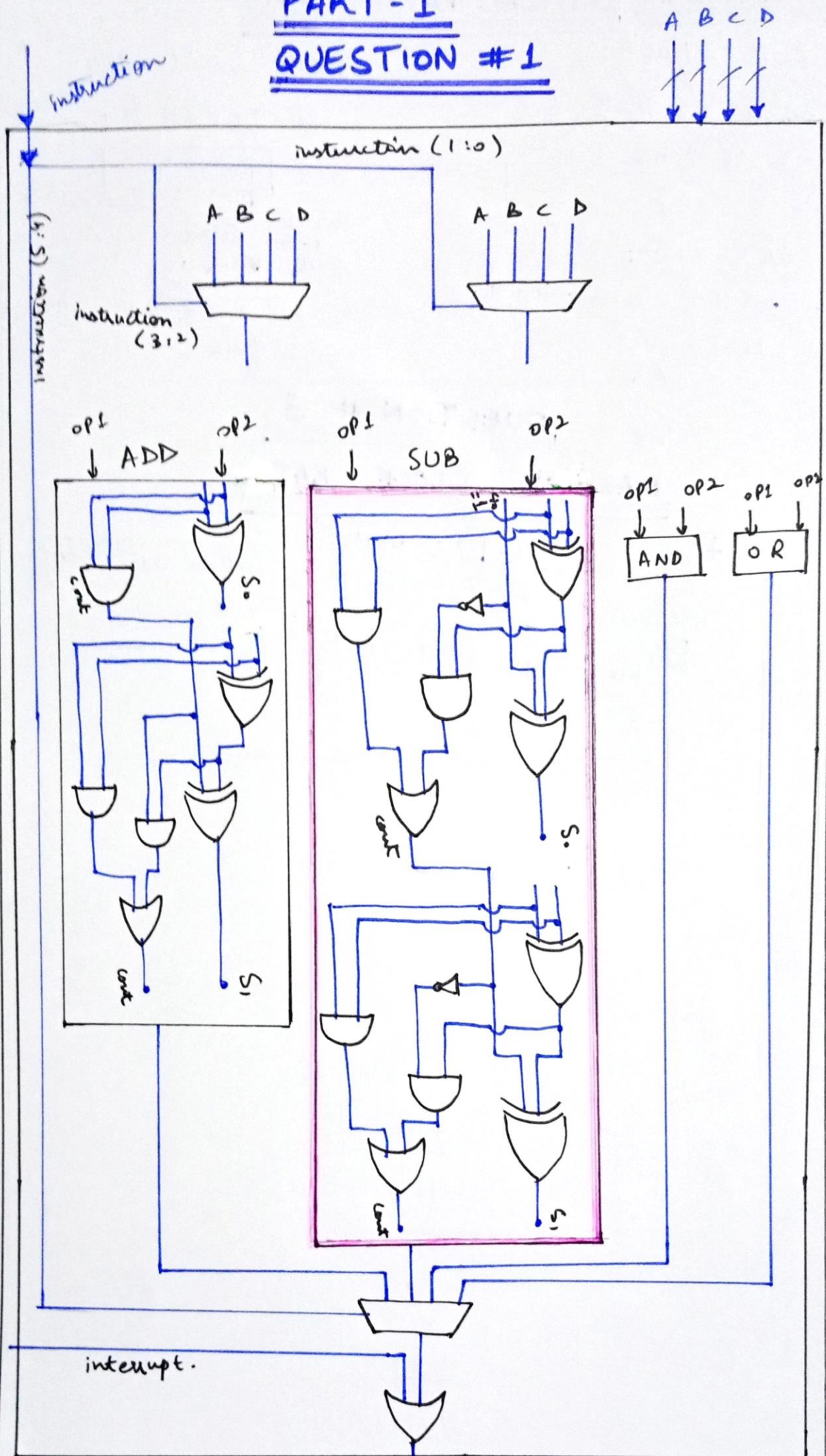

QUESTION #2 CRITICAL PATH DELAY

FOR ADDER:

$$= 0.5 + 4 + 6 + 4 + 2 + 0.3$$
$$= 16.8 \text{ ns}$$

FOR AND:

$$= 0.5 + 2 + 0.3 + 4 + 4 + 2$$
$$= 12.8 \text{ ns}$$

FOR Subtractor:

$$= 0.5 + 4 + 12 + 4 + 2 + 0.3$$
$$= \boxed{22.8 \text{ ns}}$$

Hence, this is critical path delay.

FOR XOR:

$$= 0.5 + 0.2 + 0.3 + 4 + 4 + 2$$
$$= 2.8 \text{ ns}$$


QUESTION # 3

MAXIMUM CLOCK RATE

$$t_{\text{clk_max}} = \frac{1}{22.8} \text{ Hz} = \frac{1}{\text{critical path delay}}$$


$$t_{\text{clk_max}} = 43.8596 \text{ MHz.}$$

PART # 2
QUESTION # 4

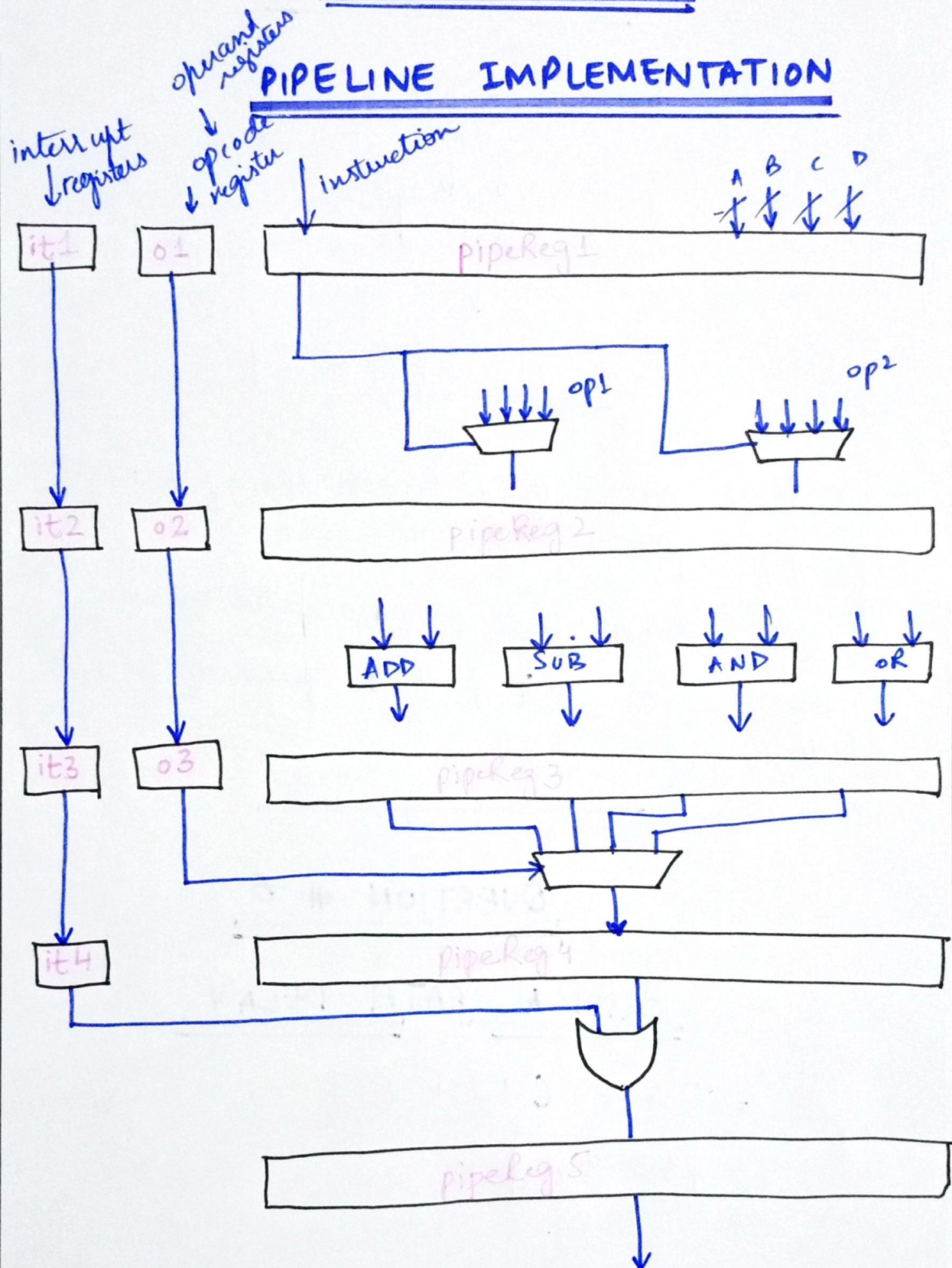

QUESTION # 5

CRITICAL PATH

 

critical path is between the pipeReg2 and pipeReg3.

SUB block full implementation is shown in Q# part I question 1 sub block.

QUESTION # 6

CRITICAL PATH DELAY

$$= 0.5 + \overset{\text{SUB}}{\uparrow} 12 + 0.3$$

$$= \boxed{12.8 \text{ ns}}$$

MAXIMUM CLOCK RATE

$$t_{clk_max} = \frac{1}{\text{critical path delay}}$$

$$= \frac{1}{12.8}$$

$$t_{clk_max} = 78.125 \text{ MHz}$$

QUESTION #7

(i)

MACHINE CODE

1. ADD B,C:

00 01 10

2. OR A,D:

11 00 11

3. SUB D,C:

01 11 10

4. AND C,D:

11 11 11

⇒ bug because
interrupt 1

(11)

BINARY CONTENTS OF REGISTERSPIPELINE INTERRUPT REGISTER

clock cycle	it1 1-bit	it2 1-bit	it3 1-bit	it4 1-bit
1	0			
2	0	0		
3	0	0	0	
4	1	0	0	0
5		1	0	0
6			1	0
7				1

PIPELINE OPERATOR REGISTERS

clock cycle	2-bit 01	2-bit 02	2-bit 03
1	00		
2	11	00	
3	01	11	00
4	10	01	11
5		10	01
6			10

PIPELINE OPERAND REGISTERS

	4-bit	4-bit	8-bit	2-bit	2-bit
clock cycle	pipeReg1	pipeReg2	pipeReg3	pipeReg4	pipeReg5
1	01 10				
2	00 11	01 10			
3	11 10	00 11	11 01 00 11		
4	10 11	11 10	11 01 00 11	11	
5		10 11	01 01 10 11	11	11
6			01 01 10 11	01	01
7				10	11
8					11